

CSE460: VLSI Design


Lecture 2

Review of digital logic design

Background


- Logic gates (AND, OR, NOT, XOR, etc.)
- Boolean algebra
- Truth tables
- Logic functions
- Logic function synthesis by
 - Sum of Products (SOP)
 - Product of Sums (POS)
 - K-maps
- Logic blocks (MUX, DEMUX)
- Sequential elements (Latch, Flip-flop)

Logic gates

 

AND

A	B	Output
0	0	0
0	1	0
1	0	0
1	1	1

 

OR

A	B	Output
0	0	0
0	1	1
1	0	1
1	1	1




XOR

A	B	Output
0	0	0
0	1	1
1	0	1
1	1	0




NOT

Input	Output
0	1
1	0

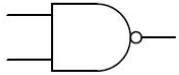


NAND

A	B	Output
0	0	1
0	1	1
1	0	1
1	1	0

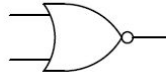

NOR


A	B	Output
0	0	1
0	1	0
1	0	0
1	1	0

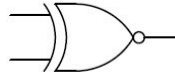



XNOR

A	B	Output
0	0	1
0	1	0
1	0	0
1	1	1


Generalized n-input logic gates

 



AND gates

  

NAND gates

 

OR gates

  

NOR gates

Axioms of Boolean Algebra

- 1a. $0 \cdot 0 = 0$
- 1b. $1 + 1 = 1$
- 2a. $1 \cdot 1 = 1$
- 2b. $0 + 0 = 0$
- 3a. $0 \cdot 1 = 1 \cdot 0 = 0$
- 3b. $1 + 0 = 0 + 1 = 1$
- 4a. If $x = 0$, then $\overline{x} = 1$
- 4b. If $x = 1$, then $\overline{x} = 0$

Boolean Algebra - Single Variable Theorems

- 5a. $x \cdot 0 = 0$
- 5b. $x + 1 = 1$
- 6a. $x \cdot 1 = x$
- 6b. $x + 0 = x$
- 7a. $x \cdot x = x$
- 7b. $x + x = x$
- 8a. $x \cdot \overline{x} = 0$
- 8b. $x + \overline{x} = 1$
- 9. $\overline{(\overline{x})} = x$

● Boolean Algebra - Two Variable Properties

- 10a. $x \cdot y = y \cdot x$
 - 10b. $x + y = y + x$
 - 11a. $x \cdot (y \cdot z) = (x \cdot y) \cdot z$
 - 11b. $x + (y + z) = (x + y) + z$
 - 12a. $x \cdot (y + z) = x \cdot y + x \cdot z$
 - 12b. $x + y \cdot z = (x + y) \cdot (x + z)$
 - 13a. $x + x \cdot y = x$
 - 13b. $x \cdot (x + y) = x$
 - 14a. $x \cdot y + x \cdot \bar{y} = x$
 - 14b. $(x + y) \cdot (x + \bar{y}) = x$
- Commutative
- Associative
- Distributive
- Absorption
- Combining

Boolean Algebra - Two & Three Variable Properties

DeMorgan's theorem

- 15a. $(x \cdot y)' = x' + y'$
- 15b. $(x + y)' = x' \cdot y'$

- 16a. $x + x' \cdot y = x + y$

- 16b. $x \cdot (x + y) = x \cdot y$

- 17a. $x \cdot y + y \cdot z + x' \cdot z = x \cdot y + x' \cdot z$ Consensus

- 17b. $(x + y) \cdot (y + z) \cdot (x' + z) = (x + y) \cdot (x' + z)$

Logic Function Synthesis - Three variable SOP & POS

- Function synthesis from truth table

Row number	x_1	x_2	x_3		Minterm	Maxterm
0	0	0	0		$m_0 = \bar{x}_1\bar{x}_2\bar{x}_3$	$M_0 = x_1 + x_2 + x_3$
1	0	0	1		$m_1 = \bar{x}_1\bar{x}_2x_3$	$M_1 = x_1 + x_2 + \bar{x}_3$
2	0	1	0		$m_2 = \bar{x}_1x_2\bar{x}_3$	$M_2 = x_1 + \bar{x}_2 + x_3$
3	0	1	1		$m_3 = \bar{x}_1x_2x_3$	$M_3 = x_1 + \bar{x}_2 + \bar{x}_3$
4	1	0	0		$m_4 = x_1\bar{x}_2\bar{x}_3$	$M_4 = \bar{x}_1 + x_2 + x_3$
5	1	0	1		$m_5 = x_1\bar{x}_2x_3$	$M_5 = \bar{x}_1 + x_2 + \bar{x}_3$
6	1	1	0		$m_6 = x_1x_2\bar{x}_3$	$M_6 = \bar{x}_1 + \bar{x}_2 + x_3$
7	1	1	1		$m_7 = x_1x_2x_3$	$M_7 = \bar{x}_1 + \bar{x}_2 + \bar{x}_3$

Logic Function Synthesis - 2/3/4 variable k-map

- Function synthesis using k-maps

x_1	x_2	
0	0	m_0
0	1	m_1
1	0	m_2
1	1	m_3

$x_1 \backslash x_2$	0	1
0	m_0	m_2
1	m_1	m_3

x_1	x_2	x_3	
0	0	0	m_0
0	0	1	m_1
0	1	0	m_2
0	1	1	m_3
1	0	0	m_4
1	0	1	m_5
1	1	0	m_6
1	1	1	m_7

$x_1 \backslash x_2$	00	01	11	10
0	m_0	m_2	m_6	m_4
1	m_1	m_3	m_7	m_5

$x_3 \backslash x_1 x_2$		x_1			
		00	01	11	10
x_3	00	m_0	m_4	m_{12}	m_8
	01	m_1	m_5	m_{13}	m_9
	11	m_3	m_7	m_{15}	m_{11}
	10	m_2	m_6	m_{14}	m_{10}
		x_2			
		x_4			

Logic Function Synthesis - 2/3/4 variable k-map


Function synthesis using k-maps

1. No zeros allowed.
2. No diagonals.
3. Only power of 2 number of cells in each group. ($2^0=1$, $2^1=2$, $2^2=4$, $2^3=8$, etc.)
4. Groups should be as large as possible.
5. Every 1 must be in at least one group.
6. Overlapping allowed.
7. Wrap around allowed.
8. Fewest number of groups possible.

Visit: <http://www.ee.surrey.ac.uk/Projects/Labview/minimisation/karrules.html>

Multiplexer

 - Multiple inputs, single output. Output is chosen by selector pin/s




Graphical symbol

s	f
0	w_0
1	w_1

Truth table

2x1 Multiplexer

 

Graphical symbol


s_1	s_0	f
0	0	w_0
0	1	w_1
1	0	w_2
1	1	w_3

Truth table


4x1 Multiplexer

D Latch

 - Level sensitive element
- *A positive level triggered D latch*
 - copies D to output Q, if Clock=1, else preserves the previous output
- *A negative level triggered D latch*
 - copies D to output Q, if Clock=0, else preserves the previous output



Graphical symbol

 


Clk	D	$Q(t+1)$
0	x	$Q(t)$
1	0	0
1	1	1


Characteristic table

D Latch

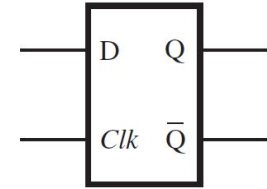- Level sensitive element
- *A positive level triggered D latch*
 - copies D to output Q, if Clock=1, else preserves the previous output
- *A negative level triggered D latch*
 - copies D to output Q, if Clock=0, else preserves the previous output



Graphical symbol

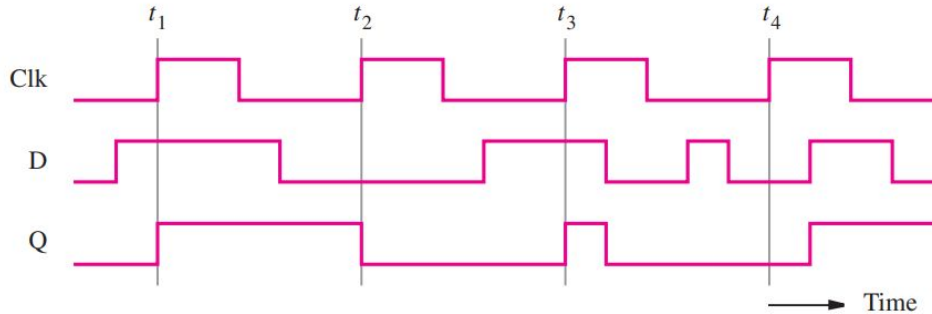

Clk	D	$Q(t+1)$
0	x	$Q(t)$
1	0	0
1	1	1




Characteristic table

D Flip-flop

- Edge sensitive element



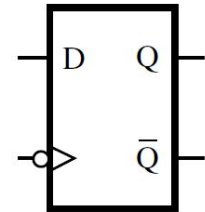
 
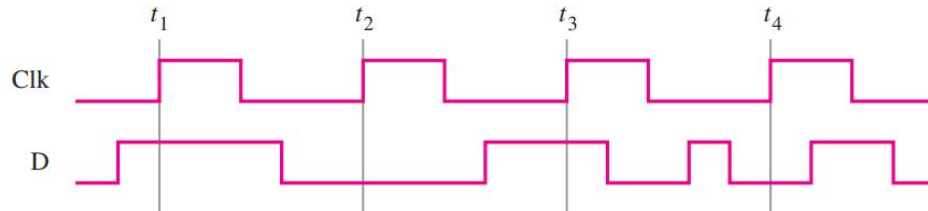
- *A positive edge triggered D flip-flop*
 - Sets $Q=D$ at all positive edges (rising edges) of the clock, retains the old value of Q otherwise
- *A negative edge triggered D flip-flop*
 - Sets $Q=D$ at all negative edges (falling edges) of the clock, retains the old value of Q otherwise



Graphical symbol




Building D Flip-flops using D Latches

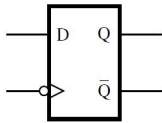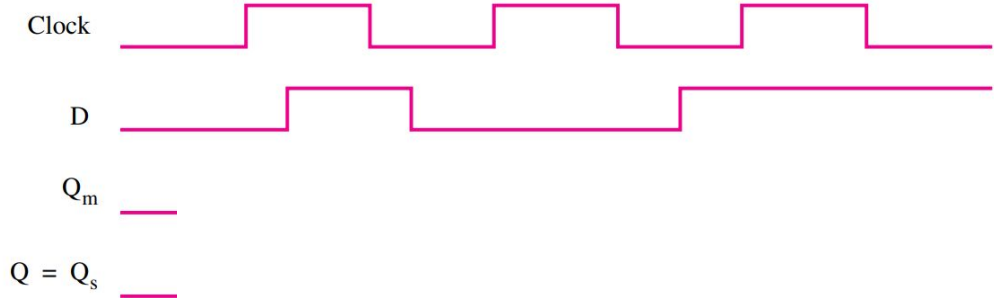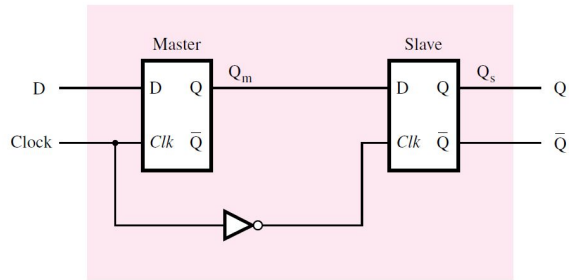- By cascading a positive level triggered D latch and a negative level triggered D latch we can build a negative edge triggered D flip-flop





Building D Flip-flops using D Latches

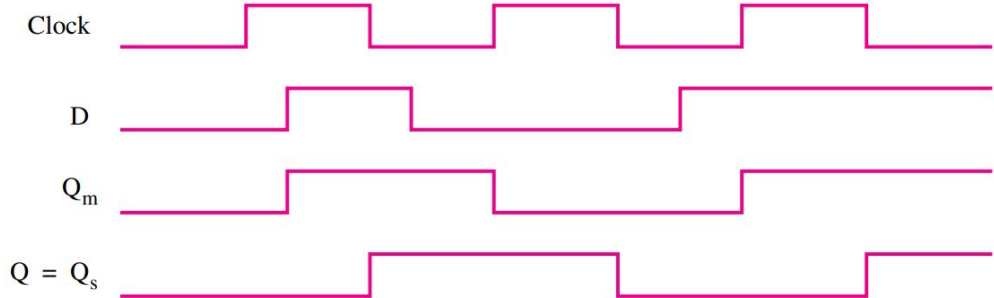 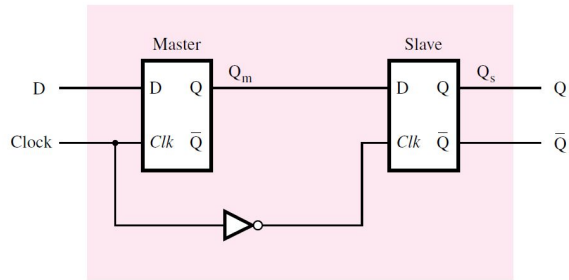- By cascading a positive level triggered D latch and a negative level triggered D latch we can build a negative edge triggered D flip-flop



Level triggered vs. Edge triggered

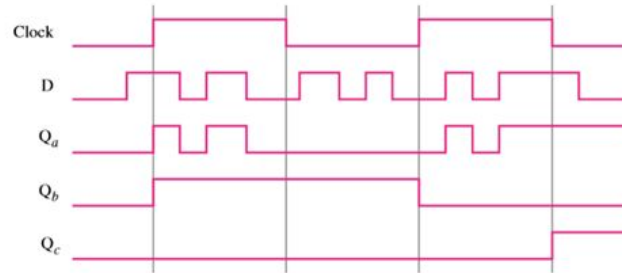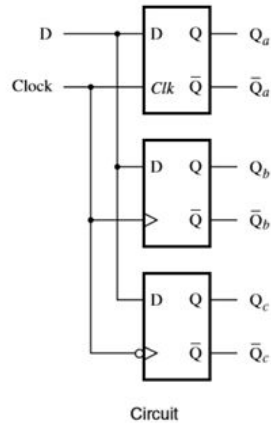- In level triggered elements
 - output is affected by the clock levels (*high/low*)
- In edge triggered elements
 - output is affected by the clock edges (positive edge/negative edge) (rising edge/falling edge)



Timing diagram

Slide references

1. <https://instrumentationtools.com/logic-gates/>
2. Stephen Brown & Zvonko Vranesic - Fundamentals of Digital Logic with Verilog Design

Thank you!