

# CSE460: VLSI Design

Lecture 7

# CMOS DC Characteristics

# Contents

- CMOS Inverter DC Characteristics
- Noise Margin
- nMOS & pMOS Pass Transistor DC Characteristics


# Static CMOS Inverter

A static CMOS inverter is built using a pMOS and an nMOS

DC Transfer function or DC response:  $V_{out}$  vs  $V_{in}$

For the CMOS inverter shown:


- $V_{in} = 0 \Rightarrow V_{out} = V_{DD}$
- $V_{in} = V_{DD} \Rightarrow V_{out} = 0$
- In between these 2 cases,  $V_{out}$  depends transistor current
- $V_{out}$  vs  $V_{in}$  relationship can be found by setting  $I_{dsn} = |I_{dsp}|$
- $V_{out}$  vs  $V_{in}$  relationship can also be found via graphical solutions

 

# CMOS Inverter DC Response

CMOS Inverter DC response can be determined as:


1. Divide the input into 5 different regions:
  - a. **A:**  $0 \leq V_{in} < V_{tn}$
  - b. **B:**  $V_{tn} \leq V_{in} < V_{DD}/2$
  - c. **C:**  $V_{in} = V_{DD}/2$
  - d. **D:**  $V_{DD}/2 < V_{in} \leq V_{DD} - |V_{tp}|$
  - e. **E:**  $V_{in} > V_{DD} - |V_{tp}|$
2. Determine the operating regions of the devices
  - a. Cutoff, Linear or Saturation?
3. Approximate  $V_{out}$  at **A**, **B**, **C**, **D** & **E** regions depending on the **pMOS** and **nMOS operating regions**

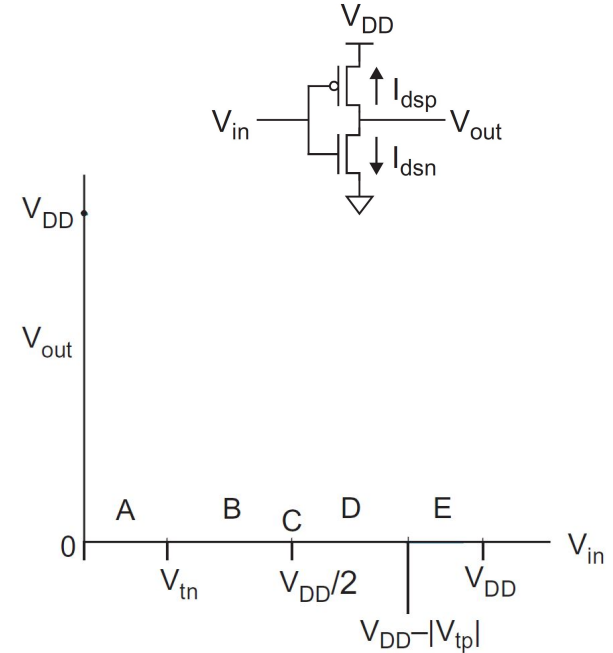

# CMOS Inverter DC response

## Region A


Region	Condition	p-device	n-device	Output
A	$0 \leq V_{in} < V_{tn}$	linear	cutoff	$V_{out} = V_{DD}$
B	$V_{tn} \leq V_{in} < V_{DD}/2$	linear	saturated	$V_{out} > V_{DD}/2$
C	$V_{in} = V_{DD}/2$	saturated	saturated	$V_{out}$ drops sharply
D	$V_{DD}/2 < V_{in} \leq V_{DD} -  V_{tp} $	saturated	linear	$V_{out} < V_{DD}/2$
E	$V_{in} > V_{DD} -  V_{tp} $	cutoff	linear	$V_{out} = 0$

 

# CMOS Inverter DC response

## Region B


Region	Condition	p-device	n-device	Output
A	$0 \leq V_{in} < V_{tn}$	linear	cutoff	$V_{out} = V_{DD}$
B	$V_{tn} \leq V_{in} < V_{DD}/2$	linear	saturated	$V_{out} > V_{DD}/2$
C	$V_{in} = V_{DD}/2$	saturated	saturated	$V_{out}$ drops sharply
D	$V_{DD}/2 < V_{in} \leq V_{DD} -  V_{tp} $	saturated	linear	$V_{out} < V_{DD}/2$
E	$V_{in} > V_{DD} -  V_{tp} $	cutoff	linear	$V_{out} = 0$

 

# CMOS Inverter DC response

## Region C

Region	Condition	p-device	n-device	Output
A	$0 \leq V_{in} < V_{tn}$	linear	cutoff	$V_{out} = V_{DD}$
B	$V_{tn} \leq V_{in} < V_{DD}/2$	linear	saturated	$V_{out} > V_{DD}/2$
C	$V_{in} = V_{DD}/2$	saturated	saturated	$V_{out}$ drops sharply
D	$V_{DD}/2 < V_{in} \leq V_{DD} -  V_{tp} $	saturated	linear	$V_{out} < V_{DD}/2$
E	$V_{in} > V_{DD} -  V_{tp} $	cutoff	linear	$V_{out} = 0$

 




# CMOS Inverter DC response

## Region D


Region	Condition	p-device	n-device	Output
A	$0 \leq V_{in} < V_{tn}$	linear	cutoff	$V_{out} = V_{DD}$
B	$V_{tn} \leq V_{in} < V_{DD}/2$	linear	saturated	$V_{out} > V_{DD}/2$
C	$V_{in} = V_{DD}/2$	saturated	saturated	$V_{out}$ drops sharply
D	$V_{DD}/2 < V_{in} \leq V_{DD} -  V_{tp} $	saturated	linear	$V_{out} < V_{DD}/2$
E	$V_{in} > V_{DD} -  V_{tp} $	cutoff	linear	$V_{out} = 0$

 

# CMOS Inverter DC response

## Region E


Region	Condition	p-device	n-device	Output
A	$0 \leq V_{in} < V_{tn}$	linear	cutoff	$V_{out} = V_{DD}$
B	$V_{tn} \leq V_{in} < V_{DD}/2$	linear	saturated	$V_{out} > V_{DD}/2$
C	$V_{in} = V_{DD}/2$	saturated	saturated	$V_{out}$ drops sharply
D	$V_{DD}/2 < V_{in} \leq V_{DD} -  V_{tp} $	saturated	linear	$V_{out} < V_{DD}/2$
E	$V_{in} > V_{DD} -  V_{tp} $	cutoff	linear	$V_{out} = 0$

 

# CMOS Inverter DC response

Complete  $V_{out}$  vs  $V_{in}$



Region	Condition	p-device	n-device	Output
A	$0 \leq V_{in} < V_{tn}$	linear	cutoff	$V_{out} = V_{DD}$
B	$V_{tn} \leq V_{in} < V_{DD}/2$	linear	saturated	$V_{out} > V_{DD}/2$
C	$V_{in} = V_{DD}/2$	saturated	saturated	$V_{out}$ drops sharply
D	$V_{DD}/2 < V_{in} \leq V_{DD} -  V_{tp} $	saturated	linear	$V_{out} < V_{DD}/2$
E	$V_{in} > V_{DD} -  V_{tp} $	cutoff	linear	$V_{out} = 0$

 
  
# Practical CMOS Inverter DC response

In reality, the sharp change at region C is not that sharp and has finite slope

- Theoretical inverter DC response vs Practical inverter DC response






# Supply Current

If  $I_{DD} = I_{dsn} = |I_{dsp}|$  is the supply current drawn from  $V_{DD}$

- $I_{DD}$  is non-zero in regions B, C & D
- $I_{DD}$  is zero in regions A & E

Region	Condition	p-device	n-device
A	$0 \leq V_{in} < V_{tn}$	linear	cutoff
B	$V_{tn} \leq V_{in} < V_{DD}/2$	linear	saturated
C	$V_{in} = V_{DD}/2$	saturated	saturated
D	$V_{DD}/2 < V_{in} \leq V_{DD} -  V_{tp} $	saturated	linear
E	$V_{in} > V_{DD} -  V_{tp} $	cutoff	linear

   

# Power Consumption


If  $I_{DD} = I_{dsn} = |I_{dsp}|$  is the current drawn from supply  $V_{DD}$

- $I_{DD}$  is non-zero in regions B, C & D
- $I_{DD}$  is zero in regions A & E

That is why we always try to work with strong signals

- A strong 0 falls in the region A where  $I_{DD} \approx 0$
- A strong 1 falls in the region E where  $I_{DD} \approx 0$

 $I_{DD} \approx 0$  or low implies low power consumption!



# Power Consumption


If  $I_{DD} = I_{dsn} = |I_{dsp}|$  is the current drawn from supply  $V_{DD}$

- $I_{DD}$  is non-zero in regions B, C & D
- $I_{DD}$  is zero in regions A & E

That is also why we try to avoid degraded signals

- A degraded 0 falls in the region B/C where  $I_{DD} \neq 0$
- A degraded 1 falls in the region D/C where  $I_{DD} \neq 0$

 $I_{DD} \neq 0$  or high implies high power consumption!



# Beta Ratio Effects


The crossover point, where  $V_{in} = V_{out}$  is called the input threshold,  $V_{inv}$

For  $\beta_p = \beta_n$ , the inverter threshold voltage,  $V_{inv} = V_{DD}/2$

$\beta_p / \beta_n$  is called the beta ratio;  $r = \beta_p / \beta_n$

- $r = 1 \Rightarrow$  inverter is un-skewed
- $r > 1 \Rightarrow$  inverter is HI-skewed
- $r < 1 \Rightarrow$  inverter is LO-skewed

 Thus, by changing  $r$  we can shift the response!






# Beta Ratio Effects for a Static CMOS Inverter

We would like to know how  $V_{inv}$  changes for a CMOS inverter as we change  $r$

For the CMOS inverter shown:

- $V_{gsp} = V_{in} - V_{DD}$
- $V_{dsp} = V_{out} - V_{DD}$
- $V_{gsn} = V_{in} - 0 = V_{in}$
- $V_{dsn} = V_{out} - 0 = V_{out}$

Assume:  $V_{tp} = -V_{tn}$

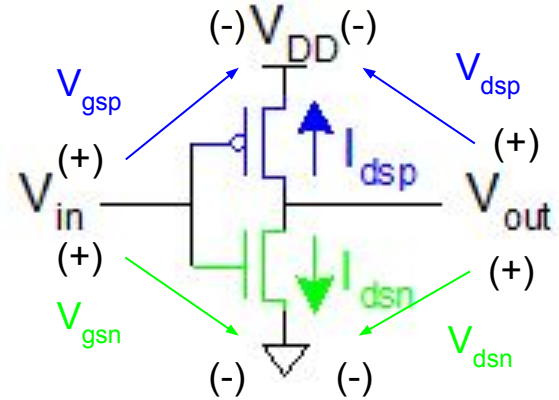

# Beta Ratio Effects for a Static CMOS Inverter

For  $\beta_p \neq \beta_n$ , we can calculate the inverter threshold voltage by setting  $V_{in} = V_{inv}$

1. In region C, both pMOS & nMOS are saturated
2. So the nMOS and pMOS currents are:


- $I_{dsp} = \beta_p (V_{gsp} - V_{tp})^2 / 2 = \beta_p (V_{inv} - V_{DD} - V_{tp})^2 / 2$

- $I_{dsn} = \beta_n (V_{gsn} - V_{tn})^2 / 2 = \beta_n (V_{inv} - V_{tn})^2 / 2$

3. Set the currents  $I_{dsp} = -I_{dsn}$

 4. Solve for  $V_{inv}$ :


$$V_{inv} = \frac{V_{DD} + V_{tp} + V_{tn} \sqrt{\frac{1}{r}}}{1 + \sqrt{\frac{1}{r}}}$$


 
# Beta Ratio Effects

So thus for  $\beta_p \neq \beta_n$ , we can calculate the inverter threshold voltage as a function of “ $r$ ”, where  $r = \beta_p / \beta_n$

$$V_{\text{inv}} = \frac{V_{DD} + V_{tp} + V_{tn} \sqrt{\frac{1}{r}}}{1 + \sqrt{\frac{1}{r}}}$$



# Other CMOS Gates

DC transfer characteristics of other static CMOS gates can be understood by collapsing the gates into an equivalent inverter

- **Series transistors** can be viewed as a single transistor of greater length
- If only one of several **parallel transistors** is ON, the other transistors can be ignored
- If several **parallel transistors** are ON, the collection can be viewed as a single transistor of greater width

# Noise Margin (Noise Immunity)

Noise margin is closely related to the DC voltage characteristics

Helps determine the allowable noise voltage on the input of a gate so that the output will not be corrupted

The specification most commonly used to describe noise margin uses two parameters:

1. The LOW noise margin,  $NM_L$
2. The HIGH noise margin,  $NM_H$

# Noise Margin

Voltage definitions:

$V_{IH}$  = minimum HIGH input voltage


$V_{IL}$  = maximum LOW input voltage

$V_{OH}$  = minimum HIGH output voltage

$V_{OL}$  = maximum LOW output voltage

$NM_L$  = The LOW noise margin


$NM_H$  = The HIGH noise margin

 

# Low Noise Margin

- The **LOW** noise margin ( $NM_L$ ) is the difference in maximum LOW input voltage recognized by the receiving gate and the maximum LOW output voltage produced by the driving gate


$$NM_L = V_{IL} - V_{OL}$$

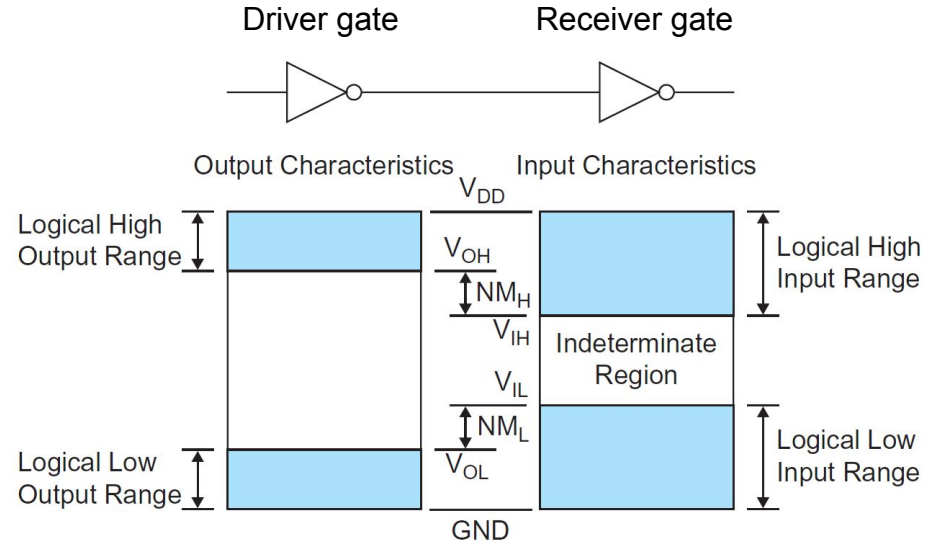

# High Noise Margin

- The **HIGH** noise margin ( $NM_H$ ) is the difference between the minimum HIGH output voltage of the driving gate and the minimum HIGH input voltage recognized by the receiving gate

$$NM_H = V_{OH} - V_{IH}$$

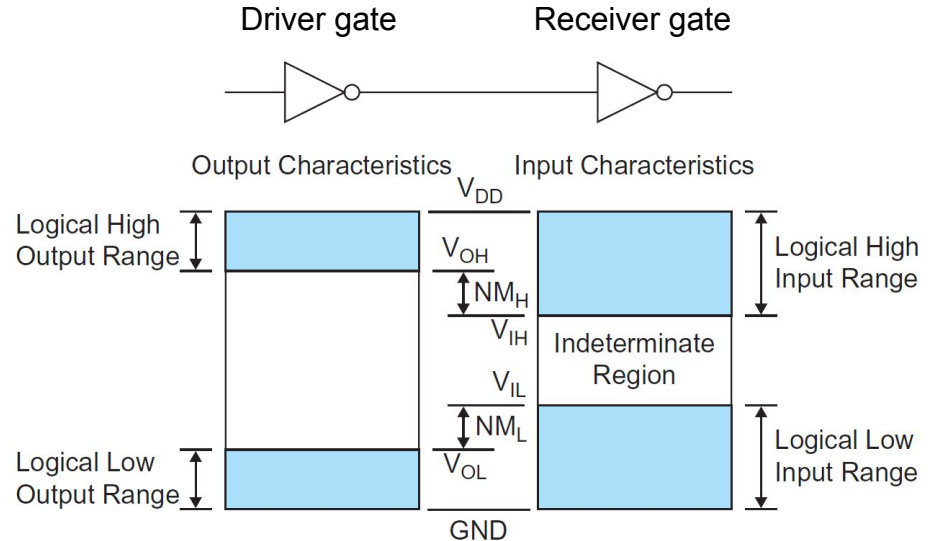




# Selecting $V_{IL}$ , $V_{IH}$ , $V_{OL}$ & $V_{OH}$

How to choose the logic levels  $V_{IL}$ ,  $V_{IH}$ ,  $V_{OL}$  &  $V_{OH}$  such that the noise margins  $NM_L$  &  $NM_H$  are maximized?


- Use the DC transfer characteristics!

 
 
# Selecting $V_{IL}$ , $V_{IH}$ , $V_{OL}$ & $V_{OH}$

How to choose the logic levels  $V_{IL}$ ,  $V_{IH}$ ,  $V_{OL}$  &  $V_{OH}$  such that the noise margins  $NM_L$  &  $NM_H$  are maximized?


- Use the DC transfer characteristics!
- Logic levels are defined at the unity gain point where the slope is  $-1$
- This gives a conservative bound on the worst case static noise margin



# Selecting $V_{IL}$ , $V_{IH}$ , $V_{OL}$ & $V_{OH}$


Logic levels of typical 5 V and 3.3 V logic families

Logic Family	$V_{DD}$	$V_{IL}$	$V_{IH}$	$V_{OL}$	$V_{OH}$
TTL	5 (4.75–5.25)	0.8	2.0	0.4	2.4
CMOS	5 (4.5–6)	1.35	3.15	0.33	3.84
LVTTL	3.3 (3–3.6)	0.8	2.0	0.4	2.4
LVC MOS	3.3 (3–3.6)	0.9	1.8	0.36	2.7

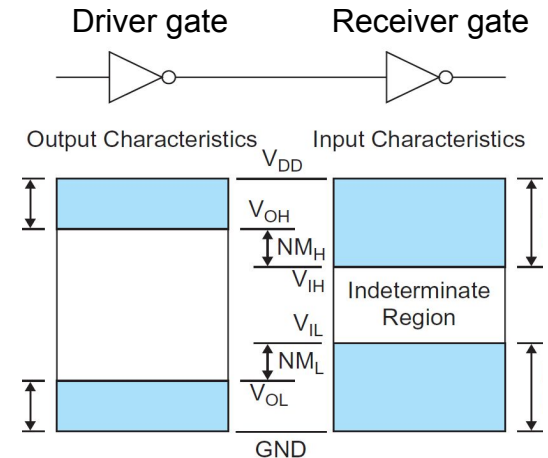
 
# Noise Margin: Summary


- **$NM_L$  or  $NM_H$  too small:** the gate may be disturbed by noise that occurs on the inputs
- **An unskewed gate has equal noise margins:** which maximizes immunity to arbitrary noise sources
- **If a gate sees more noise in the high or low input state:** the gate can be skewed to improve that noise margin at the expense of the other


 
# Noise Margin: Summary

- **Noise sources tend to scale with the supply voltage:** so noise margins are best given as a fraction of the supply voltage; for example  $0.3V_{DD}$

A noise margin of 0.4 V is quite comfortable in a 1.8 V process, but marginal in a 5 V process



# Pass Transistor DC Characteristics

Recall from our previous lectures that


- **nMOS** transistors pass '0's well but '1's poorly
- **pMOS** transistors pass '1's well but '0's poorly

We are now better prepared to define how “poorly”
 
# nMOS Pass Transistor DC Characteristics

To keep an nMOS transistor ON, we need


- $V_{gs} \geq V_{tn}$
- $\Rightarrow V_g - V_s \geq V_{tn}$
- $\Rightarrow V_s \leq V_g - V_{tn}$
- $\Rightarrow \mathbf{V_{s(max)} = V_g - V_{tn}}$



# nMOS Pass Transistor DC Characteristics

To keep an nMOS transistor ON, we need

- $V_{s(\max)} = V_g - V_{tn}$

 

nMOS transistors passing '1' ( $V_{in} = V_{DD}$ ;  $V_{out} = ?$ )

- Gate is connected to  $V_{DD}$ :  $V_g = V_{DD}$
- Current flowing from drain to source
- $V_{in} = V_d = V_{DD}$ ;  $V_{out} = V_s = ?$
- But we know  $V_{s(\max)} = V_g - V_{tn} \Rightarrow V_{out(\max)} = V_{DD} - V_{tn}$


**nMOS transistors attempting to pass a '1' never pass above  $V_{DD} - V_{tn}$**



# pMOS Pass Transistor DC Characteristics

To keep a pMOS transistor ON, we need

- $V_{sg} \geq |V_{tp}|$
- $\Rightarrow V_s - V_g \geq |V_{tp}|$
- $\Rightarrow V_s \geq V_g + |V_{tp}|$
- $\Rightarrow \mathbf{V_{s(min)} = V_g + |V_{tp}|}$

 


# pMOS Pass Transistor DC Characteristics

To keep a pMOS transistor ON, we need

- $V_{s(\min)} = V_g + |V_{tp}|$

pMOS transistors passing '0' ( $V_{in} = 0$ ;  $V_{out} = ?$ )

- Gate is connected to GND:  $V_g = 0$
- Current flowing from source to drain
- $V_{in} = V_d = 0$ ;  $V_{out} = V_s = ?$
- But we know  $V_{s(\min)} = V_g + |V_{tp}| \Rightarrow V_{out(\min)} = |V_{tp}|$

 


**pMOS transistors attempting to pass a '0' never pass lower than  $|V_{tp}|$**
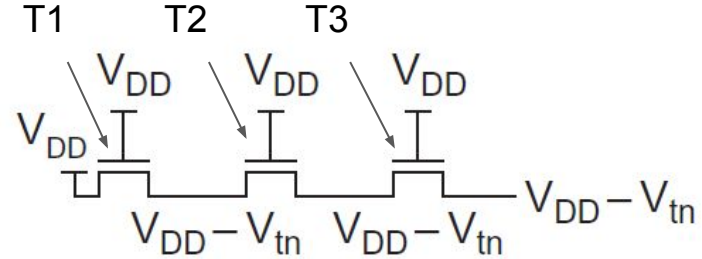
# nMOS Pass Transistor DC Characteristics

Series nMOS transistors passing '1' ( $V_{DD}$ )

- If all of the transistors have gates tied to  $V_{DD}$
- $V_{g(T1)} = V_{g(T2)} = V_{g(T3)} = V_{DD}$
- $V_{in(T1)} = V_{DD}$ ;  $V_{out(T3)} = ?$



1. Output of Transistor T1:  $V_{out(max), T1} = V_{g(T1)} - V_{tn(T1)} = V_{DD} - V_{tn}$
2. Output of Transistor T2:  $V_{out(max), T2} = V_{g(T2)} - V_{tn(T2)} = V_{DD} - V_{tn}$
3. Output of Transistor T3:  $V_{out(max), T3} = V_{g(T3)} - V_{tn(T3)} = V_{DD} - V_{tn}$

# nMOS Pass Transistor DC Characteristics


nMOS transistor driven by degraded output

- If T1 transistor has gate tied to  $V_{DD}$
- $V_{g(T1)} = V_{DD}$ ;  $V_{in} = V_{DD}$ ;  $V_{out} = ?$

Output of Transistor T1:  $V_{out(max), T1} = V_{g(T1)} - V_{tn(T1)} = V_{DD} - V_{tn}$

- Output of transistor T1 is now driving the gate of transistor T2
- T2 transistor has gate tied to  $V_{DD} - V_{tn}$
- $V_{g(T2)} = V_{DD} - V_{tn}$ ;  $V_{in} = V_{DD}$ ;  $V_{out} = ?$

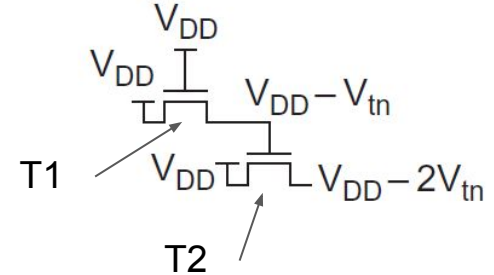
Output of Transistor T2:  $V_{out(max), T2} = V_{g(T2)} - V_{tn(T2)} = (V_{DD} - V_{tn}) - V_{tn} = V_{DD} - 2V_{tn}$



# Pass Transistor DC Characteristics: Summary

 
## nMOS pass transistor

- $V_{in} = \text{GND} \Rightarrow V_{out} = \text{GND}$  (strong 0)
- $V_{in} = V_{DD} \Rightarrow V_{out(max)} = V_g - V_{tn}$  (degraded 1)



## pMOS pass transistor

- $V_{in} = \text{GND} \Rightarrow V_{out(min)} = |V_{tp}|$  (degraded 0)
- $V_{in} = V_{DD} \Rightarrow V_{out} = V_{DD}$  (strong 1)

 

# Pass Transistor DC Characteristics: Summary

- nMOS/pMOS pass transistors sometimes produce degraded outputs
- The loss is sometimes called a threshold drop
- In old processes where  $V_{DD}$  was high and  $V_t$  was a small fraction of  $V_{DD}$ , the threshold drop was tolerable
- In modern processes  $V_{DD}$  is significantly lower and  $V_t$  is almost  $\frac{1}{3}$  of  $V_{DD}$ , the threshold drop can produce an invalid or marginal logic at the output

To solve this problem we use CMOS transmission gates

Thank You!