

## **Lecture 4:**

# **CMOS**










## **Implementation of logic blocks and sequential elements**

# Signal Strength

- ☐ *Strength* of signal
  - How close it approximates ideal voltage source
- ☐  $V_{DD}$  and GND rails are strongest 1 and 0
- ☐ nMOS pass strong 0
  - But degraded or weak 1
- ☐ pMOS pass strong 1
  - But degraded or weak 0
- ☒ Thus **nMOS** are best for pull-down network
- ☒ And, **pMOS** are best for pull-up network


# Pass Transistors

- Transistors can be used as switches

    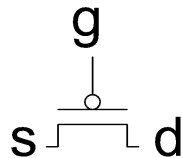 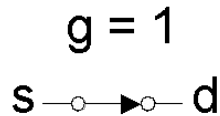  
 
# Transmission Gates



- ❑ Pass transistors produce degraded outputs
- ❑ *Transmission gates* pass both 0 and 1 well



# Tristates


□ *Tristate buffer* produces Z when not enabled

EN	A	Y
0	0	Z
0	1	Z
1	0	0
1	1	1

  

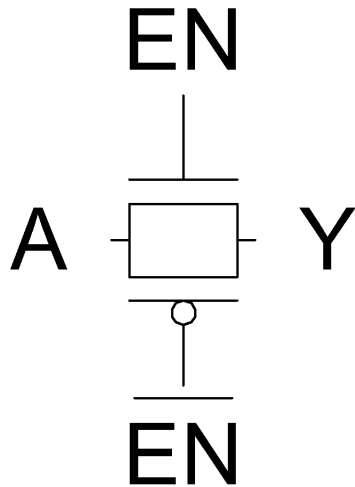
# Nonrestoring Tristate

- ❑ Transmission gate acts as tristate buffer
  - Only two transistors
  - But *nonrestoring*
    - Noise on A is passed on to Y


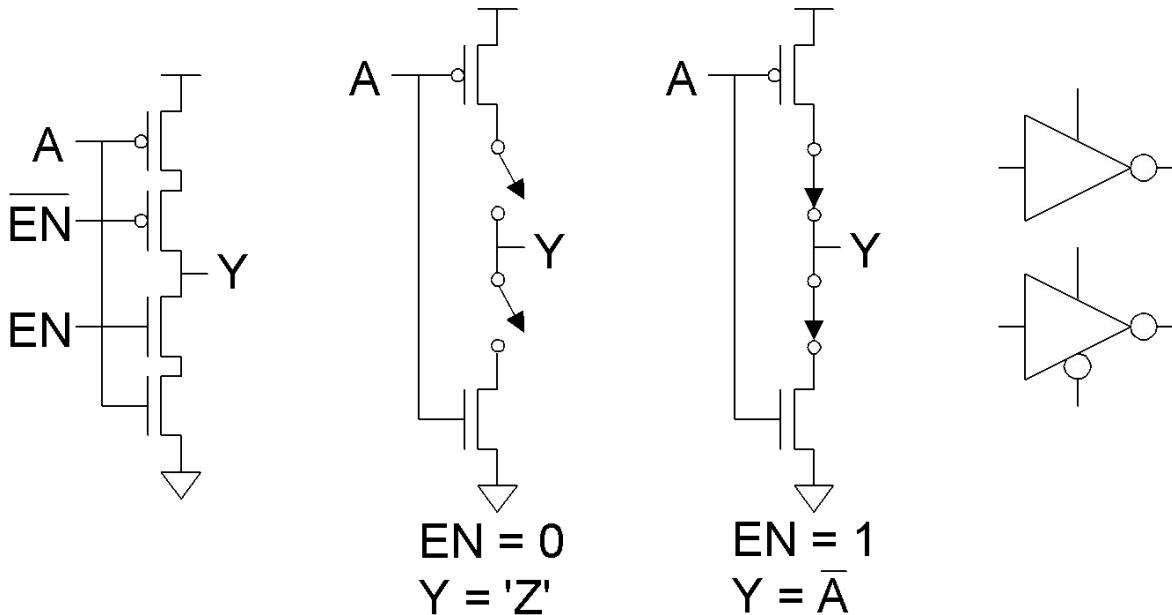
# Tristate Inverter


- ✓ ☒ Tristate inverter produces restored output
  - Violates conduction complement rule
  - Because we want a Z output



# Multiplexers

- 2:1 multiplexer chooses between two inputs

S	D1	D0	Y
0	X	0	
0	X	1	
1	0	X	
1	1	X	

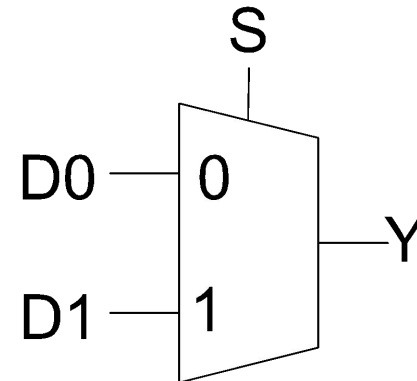




# Gate-Level Mux Design

- ❑  $Y = SD_1 + \overline{S}D_0$  (too many transistors)
- ❑ How many transistors are needed? 10

# Transmission Gate Mux




- ✓ ☐ Nonrestoring mux uses two transmission gates
  - Only 4 transistors

S	Y
0	D <sub>0</sub>
1	D <sub>1</sub>

 

 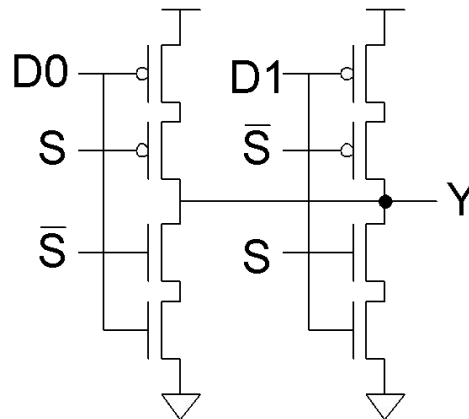
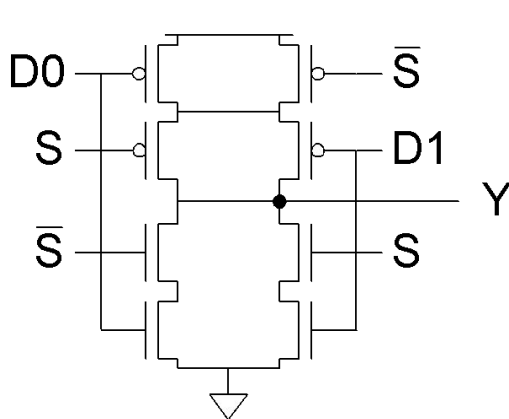
# Inverting Mux

- ❑ Inverting multiplexer
  - Use compound AOI22
  - Or pair of tristate inverters
  - Essentially the same thing
- ❑ Noninverting multiplexer adds an inverter



# 4:1 Multiplexer

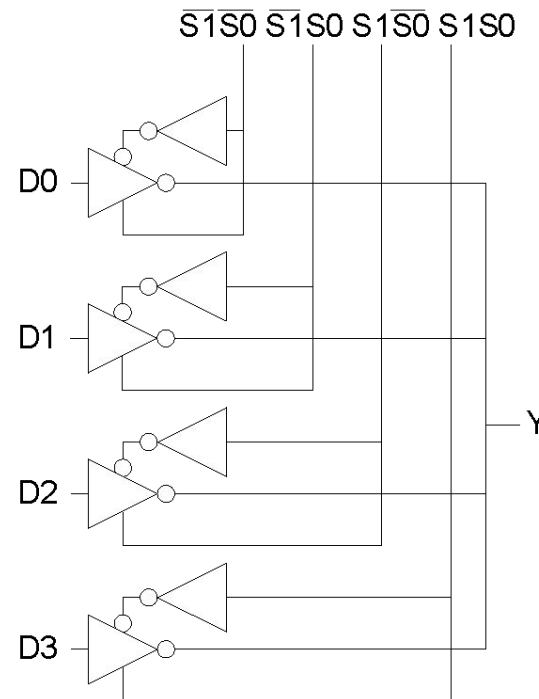
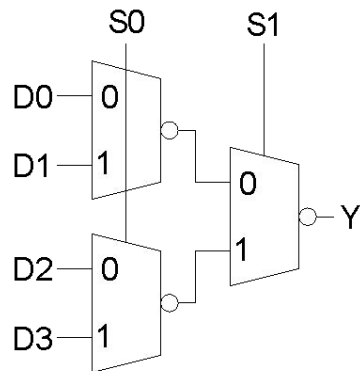
- 4:1 mux chooses one of 4 inputs using two selects
- ✓ – Two levels of 2:1 muxes
- ✓ – Or four tristates





 
 
# D Latch

- ✓ ☒ When  $\text{CLK} = 1$ , latch is *transparent*
  - D flows through to Q like a buffer
- ✓ ☒ When  $\text{CLK} = 0$ , the latch is *opaque*
  - Q holds its old value independent of D
- ☐ a.k.a. *transparent latch* or *level-sensitive latch*






# D Latch Design

- ✓ ☒ Multiplexer chooses D or old Q

  

# D Latch Operation

  
 



  
# D Flip-flop


+ve edge triggered

- ❑ When CLK rises, D is copied to Q
- ❑ At all other times, Q holds its value
- ❑ a.k.a. *positive edge-triggered flip-flop, master-slave flip-flop*



# D Flip-flop Design

- Built from master and slave D latches

 

# D Flip-flop Operation

